

Duration: 3hrs

Max. Marks: 80

- N.B. : (1) Question No. 1 is compulsory.
- (2) Solve any **three** questions from the **remaining five**
- (3) Figures to the right indicate full marks
- (4) Assume suitable data if necessary and mention the same in answer sheet.

**Q No.1** Attempt **any 5** questions

- Compare Depletion and Enhancement MOSFET. **5**
- Why LC oscillators are preferred for high frequency applications. **5**
- Draw small signal model of JFET & explain each parameter. **5**
- Write down current equation of diode and explain significance of each parameters. **5**
- State and explain Barkhausen's criteria for oscillations. **5**
- Find Q point for the following circuit shown in fig.1. Assume  $\beta=100$  and  $V_{BE}=0.6V$  **5**

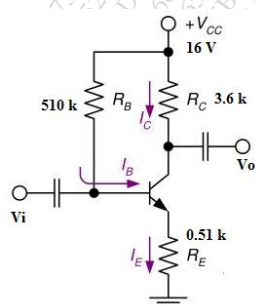


Fig.1

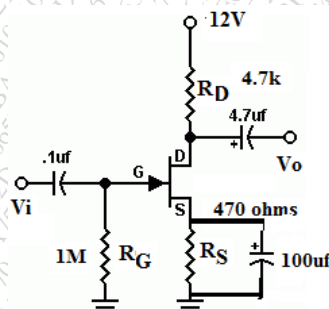


Fig.2

- Q No.2**
- Explain the working of wein bridge oscillator and derive the expression for frequency of oscillation. **10**
  - Derive the expression for voltage gain, Current gain, Input impedance and output impedance for bypassed voltage divider CE BJT amplifier. **10**

- Q No.3**
- Explain Construction and operation of varactor diode. **10**
  - For JFET amplifier shown in fig.2, find  $A_v$ ,  $R_i$ ,  $R_o$ . Assume FET parameters:  $I_{DSS}=8mA$ ,  $V_P = -3V$ ,  $r_d = 100k\Omega$  **10**

**Q  
No.4**

- a Determine  $A_v$ ,  $A_i$ ,  $R_i$ ,  $R_o$  for unbypassed BJT amplifier shown in fig.3. **10**  
Assume  $\beta=120$  and  $V_{BE}=0.6V$ .

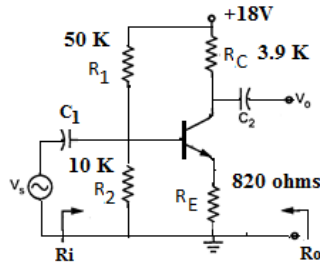


Fig.3

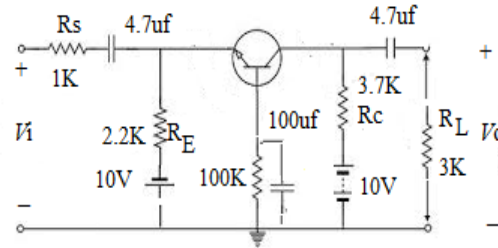


Fig.4

- b For the circuit shown in fig.4 Determine voltage gain, Input and output impedance. Assume  $\beta=120$  and  $V_{BE}=0.7V$ . **10**

**Q  
No.5**

- a For MOSFET amplifier shown fig 5 . Determine  $A_v$ ,  $Z_i$ ,  $Z_o$  . Assume MOSFET DATA:  $K_N = 1 \text{ MA/V}^2$ ,  $V_{TN} = 0.7 \text{ v}$  (10 M)

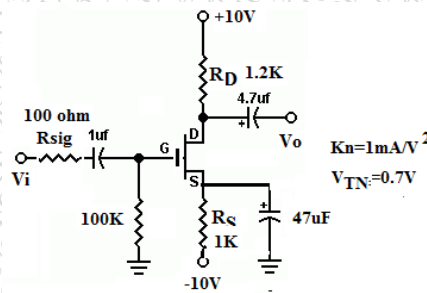


Fig.5

- b Define stability factor. Derive the expression for stability factor of voltage divider bias. Explain which biasing technique is more stable.

**Q  
No.6** Write short notes on (any Two)

- a D.C. load line & significance of Q pt. **10**  
b Clipping Circuit **10**  
c Comparison of BJT CE & JFET CS Amplifier **10**

\*\*\*\*\*