

S.E. (Computer) (Sem-III) (CBCSGS)

Date-14/5/19

(3 Hours)

[Total Marks : 80]

N.B. : 1. Question **ONE** is **Compulsory**.

2. Solve any **THREE** out of remaining.

3. **Draw** neat and **clean** Diagrams.

4. Assume suitable **data** if required

Q.1. Attempt the following

- a) Explain the concept of virtual ground in op-amp 5
- b) Explain block diagram of PCM 5
- c) Compare FET and BJT 5
- d) What is ZCD? 5

Q.2. A. Explain the construction and working of n-channel JFET with help of characteristic curves. 10

B. Explain op-amp as integrator 10

Q.3. A. List down various parameters of op-amp with their practical values and ideal values for IC741. 10

B. Explain working of PLL as frequency multiplier with diagram. 10

Q.4. A. Explain Superheterodyne Receiver along with waveforms at each stage . 10

B. What are power amplifiers .what are the types of power amplifiers .Explain class C power amplifiers. 10

Q.5. A. Derive the equations for Z_i , Z_o , A_v for common source configuration using voltage divider network 10

B. Discuss Delta Modulation and Adaptive Delta Modulation

Q.6. Write short note: 20

- a) TDM-PCM System
- b) Generation of FM
- c) Comparators.
- d) op-amp as summing amplifier
