

(3 hours)

Marks: 80

Note the following instructions.

1. Question No.1 is compulsory
2. Attempt any three questions from remaining five questions
3. Solve in total 4 questions
4. Assume suitable data wherever necessary, justify the same
5. Figures to the right indicate full marks.

1.a Mention the different types of faults present in logic circuits and list the method to detect and locate them. [ 5]

1.b What is a Threshold logic element? Give its advantages and limitations [ 5]

1.c What is a logic hazard and describe in brief the types of logic hazard [ 5]

1.d Differentiate between Mealy and Moor type state machine. [5]

2.a Use the Quine–McCluskey method to generate the set of essential prime implicants and to obtain the minimal expressions for the following functions. [ 10]

$$T(w, x, y, z) = \sum (0, 1, 2, 8, 9, 11, 13, 15)$$

2.b In the following state table, find the equivalence partition and the corresponding reduced machine in standard form. [10]

PS	NS, z	
	x = 0	x = 1
A	F, 0	B, 1
B	G, 0	A, 1
C	B, 0	C, 1
D	C, 0	B, 1
E	D, 0	A, 1
F	E, 1	F, 1
G	E, 1	G, 1


3.a (i) Give the properties of symmetric function. [10]

(ii) Decomposed the following function and determine the functions F and  $\Phi$ .


$$f(v, w, x, y, z) = \sum (1, 2, 7, 9, 10, 17, 19, 26, 31) + \sum \phi (0, 15, 20, 23, 25)$$

$$= F[\Phi(v, w, y), x, z]$$

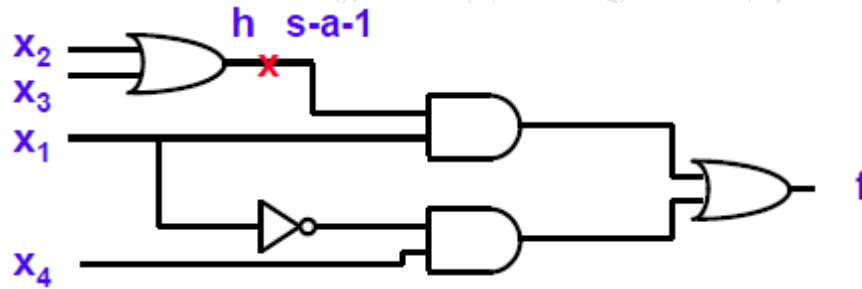- 3.b Find all the test vectors that detect input  $h$  s-a-1 by using the Path sensitization and the Boolean Differences method. [ 10]



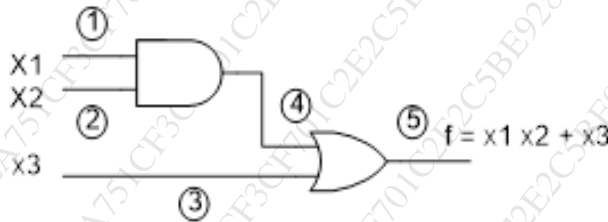- 4.a Show that threshold logic realization of Full Adder requires only two threshold elements. (Note that both sum and carry must be generated) [ 10 ]
- 4.b Explain the synthesis procedure with suitable example for the design of fundamental-mode asynchronous sequential circuits. [ 10]
- 5.a Find the fault table for all stuck-at faults of the following circuit [ 10]



- 5.b Explain the lattice of closed partitions of machine. [ 10]
6. a Draw the state diagram and the state table for Moore type sequence detector to detect the sequence 110. [ 10]
6. b Draw and explain the ASM chart for a weighing machine. [ 10]

\*\*\*\*\*