

Time: 3 HRS

Marks: 80

Note: 1. Q. No1 is compulsory

2. Solve any three questions out of the remaining five

3. Figures to right indicate full marks

4. Assume suitable data where necessary

Q.1 Solve any four

(20)

- Draw and implement EX-OR and EX-NOR GATES using NAND gates
- What is the difference between Multiplexer and De- multiplexer circuits?
- Implement Basic gate using NAND and NOR gate
- Convert $(101101.1101)_2$ to decimal, hexadecimal and octal form
- Convert JK Flip flop to D Flip Flop

Q.2

- Draw and explain various types of Shift Register with neat diagram. **(10)**
- Draw and explain Ring Counter with a neat diagram **(10)**

Q.3. a. Draw and explain Comparator IC 7485 and ALU IC 74181

(10)

b. Draw and explain data objects and types in VHDL **(10)**

Q.4. a. Implement the following Boolean function using only one 8:1 Mux and a few gates

$$F = \sum m(0, 1, 3, 4, 5, 7, 9, 11, 12, 15) \quad \textbf{(10)}$$

b. Draw and explain BCD and Excess 3 code with examples. **(10)**

Q.5. a. Design Mod 10 ripple counter using suitable Flip Flop **(10)**

b. Design and simplify using Quine – Mcclusky Method **(10)**

$$F(A,B,C,D) = \sum m(0,3,5,11,13) + d(1,2,5)$$

Q.6. Solve any four

(20)

- Perform subtraction of $(33)_{10}$ and $(44)_{10}$ using ones complement.
- Current mirror circuit
- Sequential and Combinational Circuit
- VHDL program format
- Convert SR to T Flip Flop