

(3 Hours)

Max. marks: 80

- N.B.:** (1) Question No. 1 is compulsory.
 (2) Solve any three questions from the remaining five questions.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data if necessary and mention the same in answer sheet.

- Q.1 Attempt any 5 questions. [20]
 a) Explain MOSFET as an amplifier.
 b) Compare RC coupled, transformer coupled and direct coupled.
 c) Explain the effect of source resistance on design of multistage amplifiers.
 d) Explain crossover distortion.
 e) Explain Barkhausen criterion for sustained oscillations.
 f) What are the advantages of negative feedback amplifiers?
- Q.2 a) What are the different biasing techniques used to bias D-MOSFET and E-MOSFET. Explain with the help of appropriate diagrams [10]
 b) Discuss Darlington pair. What are its primary features? Obtain expression for A_V , A_i and R_i . [10]
- Q.3 a) Design a class-B power amplifier with the following specifications: Output power = 8 W, $R_L = 8 \Omega$, $V_{CC} = 15 \text{ V}$. [10]
 b) Design a two stage RC coupled cascaded amplifier for the following specification $|A_V| \geq 500$, $R_i > 1 \text{ M}\Omega$, $S_i \leq 8$, $V_{o(\text{rms})} = 3 \text{ V}$ and $f_L = 20 \text{ Hz}$. [10]
- Q.4 a) Explain working principle of Wein Bridge oscillator. Derive the expression for its frequency of oscillation and value of gain required for sustained oscillation. [10]
 b) Draw the circuit diagram of transformer coupled class A power amplifier and derive the expression for maximum conversion efficiency. [10]
- Q.5 a) Design a two stage RC coupled CE-CE amplifier for the following parameters $A_V \geq 2500$, $f \geq 40 \text{ Hz}$, $S \leq 10$, $V_O = 2.5$. Use transistor BC147A. [10]
 b) Explain the concept of negative feedback and explain its effect on gain, input and output impedance in voltage shunt feedback network. [10]
- Q.6 Short notes on: (Attempt any four) [20]
 a) V-I characteristics of MOSFET
 b) LC oscillators
 c) Cascode amplifier
 d) Current series feedback amplifier
 e) Design of heat sink

Transistor type	P _{max} Watts @ 25°C	I _{cm} Amps @ 25°C	V _{CE} volts d.c.	V _{CE} volts d.c. (30s)	V _{CE} volts d.c. (30s)	V _{CE} volts d.c. (30s)	V _{CE} volts d.c.	V _{CE} volts d.c.	D.C. current typ. max.	Signal amp. max.	h _{FE} max.	V _{BE} max.	θ _{JA} °C/W	Derate above 25°C W/°C
2N 3055	115-5	15-0	1-1	100	60	70	90	7	20	50	120	1-8	1-5	0-7
BCN 055	50-0	5-0	1-0	60	50	55	60	5	25	50	125	1-5	3-5	0-4
ECN 149	30-0	4-0	1-0	50	40	—	—	8	30	50	115	1-2	4-0	0-3
ECN 100	5-0	0-7	0-6	70	60	65	—	6	50	90	280	0-9	35	0-03
BC147A	0-25	0-1	0-25	50	45	50	—	6	115	180	220	0-9	—	—
2N 525(PNP)	0-225	0-5	0-25	85	30	—	—	—	35	—	—	—	—	—
BC147B	0-25	0-1	0-25	50	45	50	—	6	200	290	450	0-9	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0	3-5	4-0
I _{DS} max. mA	10	9-0	8-3	7-6	6-8	6-1	5-4	4-2	3-1	2-2	2-0	1-1	0-5	0-0
I _{DS} typ. mA	7-0	6-0	5-4	4-6	4-0	3-3	2-7	1-7	0-8	0-2	0-0	0-0	0-0	0-0
I _{DS} min. mA	4-0	3-0	2-2	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0

Transistor type	A _{IC}	A _{OC}	A _{VC}	θ _{JA}
BC 147A	2-7 K Ω	18 μ Ω	1-5 × 10 ⁻⁴	0-4°C/mW
2N 525 (PNP)	1-4 K Ω	25 μ Ω	3-2 × 10 ⁻⁴	0-4°C/mW
BC 147B	4-5 K Ω	30 μ Ω	—	—
ECN 100	500 Ω	—	—	—
ECN 149	250 Ω	—	—	—
ECN 055	100 Ω	—	—	—
2N 3055	25 Ω	—	—	—

N-Channel JFET

Type	V _{GS} max. Volts	V _{GS} max. Volts	V _{GS} max. Volts	P _D max. @ 25°C	T _J max.	I _{SS}	I _{SS} (typical)	-V _P Volts	r _d	Derate above 25°C	θ _{JA}
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ A	6	50 KΩ	2 mW/°C	0-59°C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ A	2-5	50 KΩ	—	0-59°C/mW

A6770F26CF24EE77E6D958C4E143C9BI
