

Duration –Three Hrs.

Total Marks-80

N. B. 1. Question No. 1 is compulsory

2. Solve any three questions out of remaining five questions

3. Figures to the right indicate full marks

Q. 1 Attempt Any four of the followings

A Draw and explain V-I characteristics of SCR

5

B Explain the need of freewheeling diode in controlled rectifier with R-L load.

5

C Draw and explain equivalent circuit of an OP-Amp.

5

D Differentiate Between Multiplexer and De-multiplexer.

5

E Compare between DC Motor and AC Motor.

5

Q.2 A Draw and explain functional block diagram of timer IC 555.

7

B Draw and explain fan regulator circuit using TRIAC and DIAC. Draw Waveforms.

7

C State and prove Demorgan's theorems in Boolean Algebra.

6

Q.3 A Draw and explain semi-controlled rectifier. Draw waveforms.

7

B Draw and explain MSP430 architecture.

7

C Draw and explain Instrumentation amplifier State its advantages and disadvantages.

6

Q.4 A Draw and explain BLDC motor. State its advantages.

7

B State and Define specification parameters of Digital logic family.

7

C Explain construction and characteristics of Power BJT

6

Q.5 A With the help of connection diagram, derive the relation for voltage gain in inverting mode of operation of operational amplifier.

7

B With the help of circuit diagram and waveforms, explain the generation of output voltage in three phase inverter in 180° conduction mode of operation.

7

C What do you understand by servo motor. State its applications.

6

Q.6 A Draw and explain slip-torque characteristics of three phase AC motor.

7

B Draw and explain CMOS NAND gate with the help of truth table.

7

C Differentiate between microprocessor and Microcontroller.

6
