

(3 Hours)

[Max. Marks 80]

- N.B. (1) Question No. 1 is compulsory  
 (2) Assume suitable data if necessary  
 (3) Attempt any three questions from remaining questions

1

- (a) Convert  $(1762.46)_{10}$  into octal, binary and hexadecimal. (3)  
 (b) Prove OR-AND configuration is equivalent to NOR-NOR configuration. (3)  
 (c) Perform Subtraction using 16's complement. (4)  
     i)  $(CB1)_{16} - (971)_{16}$   
     ii)  $(426)_{16} - (DBA)_{16}$   
 (d) Find 8's complement of following numbers. (2)  
     i)  $(27)_8$       ii)  $(321)_8$   
 (e) Perform following subtraction  $(52)_{10} - (65)_{10}$  using 2's complement method. (2)  
 (f) Write the hamming code for 1010. (2)  
 (g) Implement the following Boolean equation using NAND gates only. (2)  
      $Y = AB + CDE + F$   
 (h) Explain the term prime implicant. (2)

- 2 (a) Design a 4-bit ripple adder. (10)  
 (b) Obtain the minimal expression using Quine Mc-Cluskey method (10)  
      $F(A,B,C,D) = \sum m(1, 5, 6, 12, 13, 14) + d(2, 4, )$

- 3 (a) Implement a full adder using 8: 1 multiplexer. (10)  
 (b) Implement the following functions using demultiplexer. (5)  
      $F1(A, B, C) = \sum m(0, 3, 7)$      $F2(A, B, C) = \sum m(1, 2, 5)$   
 (c) Simplify  $F(A, B, C, D) = \prod M(3, 4, 5, 6, 7, 10, 11, 15)$  and implement using (5)  
     minimum number of gates.

- 4 (a) Compare TTL and CMOS logic with respect to fan in, fan out, propagation delay, (5)  
     power consumption, noise margin, current and voltage parameters.  
 (b) Draw the circuit for S-R flip flop using two NOR gates and write the architecture (5)  
     body for the same using structural modelling.  
 (c) Explain 1-digit BCD Adder. (10)

- 5 (a) Convert JK flip flop to SR flip flop and D flip flop. (10)  
 (b) Design 3 bit synchronous counter using T flip flops. (10)

- 6 Write short note on (any four) (20)  
 (a) State table  
 (b) ALU IC 74181  
 (c) Sequence Generator  
 (d) Data flow modelling  
 (e) 4-bit ring counter

\*\*\*\*\*