

(3 Hours)

[Total Marks: 80

N.B.: (1) Question No. 1 is **compulsory**.

(2) Solve any **three** questions out of remaining **five**.

(3) Figures to **right** indicate **full** marks.

(4) Assume suitable **data** where **necessary**.

- Q1. Solve **any four** 20
- a) Prove that NAND and NOR gate are universal gate.
 - b) Convert following decimal number to Binary, Octal, Hexadecimal and Gray code
i) $(256)_{10}$ ii) $(45)_{10}$
 - c) Draw and explain circuit diagram of a differentiator using Op-amp.
 - d) Convert S-R flip flop to D flip flop.
 - e) Derive the relation between α and β
- Q2. a) Explain Voltage Divider Biasing Circuit with its stability factor. 10
- b) Implement following using only one 8:1 Multiplexer and few gates.
 $F(A,B,C,D) = \sum m(0,1,2,3,5,7,9,11,12,15)$ 10
- Q3. a) Draw circuit diagram and explain the operation of Astable Multivibrator using IC555. 10
- b) Design 4-bit binary to Excess-3 code conversion. 10
- Q4. a) Minimize the following four variable logic function using K-map and design by using only NAND gates 10
 $f(A,B,C,D) = \sum m(0,1,2,3,4,7,8,9,11,12,15)$
- b) What are the different methods used to improve CMRR in Differential Amplifier. Explain one in brief. 10
- Q5. a) Design a Mod 12 asynchronous counter using J-K-Flip Flop. 10
- b) With the help of neat diagram explain functioning of Universal Shift register. 10
- Q6 Write short notes on **any four** 20
- a) Design XOR gate using only NOR gates.
 - b) Explain working of a Current Mirror Circuit.
 - c) Write VHDL program for half adder.
 - d) Explain Encode and Decoder.
 - e) Explain working of Zener diode with VI characteristics.
