

Time: 3 hour

Max marks 80

- N.B.:** (1) Question 1 is compulsory.  
 (2) Attempt any 3 out of remaining 5 questions  
 (3) Assume suitable data if required.  
 (4) Figures to the right indicate full marks.

**Q1. Solve any four**

- a) Prove that NAND and NOR are universal gates 05  
 b) Why and which code is used for labelling the cells of K-map 05  
 c) Perform the following operation using 2's complement method 05  
     (i)  $(7)_{10} - (15)_{10}$  (ii)  $(50)_{10} - (2A)_{16}$   
 d) Write a VHDL code for 4-bit adder 05  
 e) What is Race around condition in JK FF how to overcome it 05

**Q 2 Solve the following**

- a) Convert SR flip flop to JK Flip flop 10  
 b) Minimize the following function using Quine MC-Cluskey 10  
 $f(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$

**Q 3 Solve the following**

- a) Using Boolean algebra prove the following  
 i)  $AB + BC + A\bar{C} = AB + A\bar{C}$  10  
 ii)  $[(C + C\bar{D})(C + C\bar{D})][AB + A\bar{B}(A \text{ XOR } B)] = C$   
 b) Convert following to decimal 10  
 (i)  $(352.7)_8$  (ii)  $(458.54)_8$

**Q .4 Solve the following**

- a) What is shift register? Explain anyone type of shift register give its applications 10  
 b) Design two-bit comparator and implement using logic gates 10

**Q 5 Solve the following**

- a) Design 3 bit binary to Gray code converter circuit using logic gates 10  
 b) Draw and explain a neat circuit diagram of BCD adder using IC 7483 10

**Q.6. Solve the following**

- a) Compare PAL with PLA 05  
 b) Represent the following by Boolean expression by min/max terms. 05  
 $Y(A, B, C, D) = (A + B + C)(\bar{A} + C + D)$   
 c) Design Full adder circuit using PLA 10

Q.P.Code:10020818

Please read as

Q.3) a) i)  $AB + BC + \bar{A}C = AB + \bar{A}C$

ii)  $[(C + \bar{C}D)(C + \bar{C}\bar{D})][AB + \bar{A}\bar{B} + (A \text{ ExOR } B)] = C$

Q.3)b) ii)  $(457.54)_8$