

[3 Hours]

[Marks: 80]

Please check whether you have got the right question paper.

- N.B:
1. Question No. 1 is compulsory.
 2. Solve any three questions out of remaining three questions.
 3. Figures to the right indicate full marks.

- | | | |
|----|---|----|
| 1. | (a) Draw and explain V-I characteristics of SCR. | 05 |
| | (b) Draw and explain equivalent circuit of an OP-AMP. | 05 |
| | (c) State and prove Demorgan's Theorems. | 05 |
| | (d) Enlist all important features of logic family circuit. | 05 |
| 2. | (a) Draw and explain slip-torque characteristics of AC motor. | 07 |
| | (b) What is GTO? Explain switching characteristics of GTO. | 07 |
| | (c) Compare DIAC and TRIAC. | 06 |
| 3. | (a) Draw and explain full controlled rectifier with R load. Draw waveforms. | 07 |
| | (b) Explain with neat diagram MSP 430 architecture. | 07 |
| | (c) Draw and explain second order low pass filter. | 06 |
| 4. | (a) Draw circuit diagram and waveforms of single phase full bridge inverter with R load. | 07 |
| | (b) Compare CMOS logic family with TTL logic family. | 07 |
| | (c) What is servo speed? Explain working principle of servo motor. | 06 |
| 5. | (a) Derive the relation for voltage gain in inverting mode in operational amplifier and compare it with non inverting mode. | 07 |
| | (b) Draw and explain R triggering method of SCR. | 07 |
| | (c) Draw and explain astable mode of operation of IC 555. | 06 |
| 6. | (a) Explain the application of piezo-electric activator drive. | 07 |
| | (b) Compare DC series motor and DC shunt motor. | 07 |
| | (c) Explain different applications of microcontroller. | 06 |