


Duration: 3hrs

[Max Marks:80]

- N.B. : (1) Question No 1 is Compulsory.  
 (2) Attempt any three questions out of the remaining five.  
 (3) All questions carry equal marks.  
 (4) Assume suitable data, if required and state it clearly.

**Q1.** All the questions are compulsory


- a. Find the value of  $V_x$  (5)

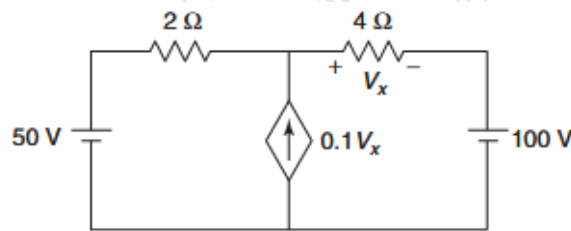


- b. The reduced incidence matrix of an oriented graph is given below. Find the possible number of trees. (5)

$$A = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

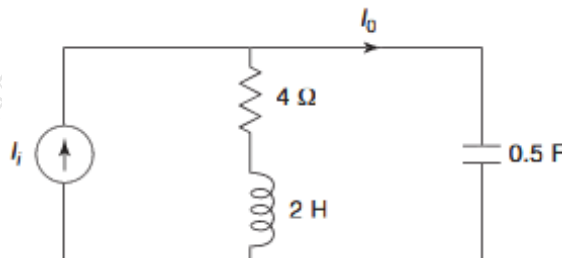- c. Draw the pole zero plot for  $I_0/I_1$  (5)



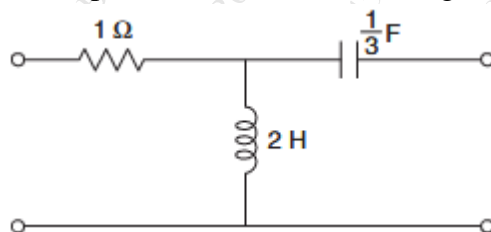
- d. Find Z parameters for the following two port network (5)



**Q2.** Solve the following


- a. Find the value of maximum power transferred to the load of  $1\Omega$

(10)

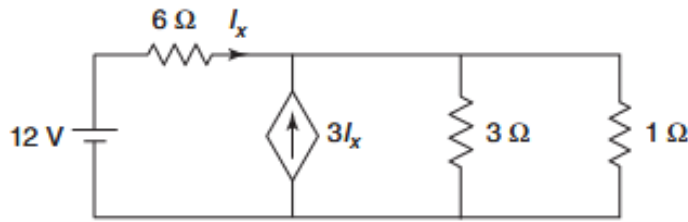

- b. Write incidence matrix, tieset matrix and cutset matrix


(10)

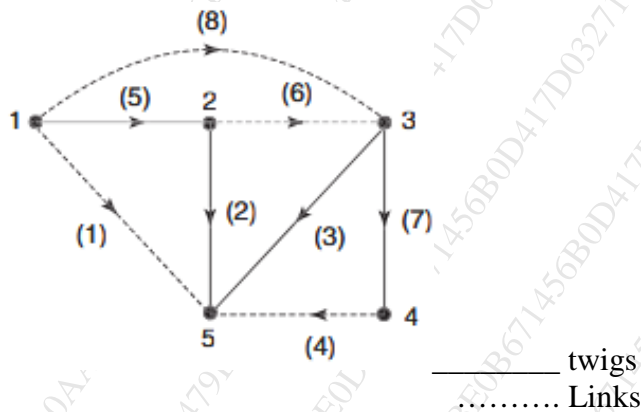

**Q3.** Solve the following


- a. The switch is changed from the position 1 to the position 2 at  $t = 0$ , steady condition having reached before switching. Find the values of  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$

(10)

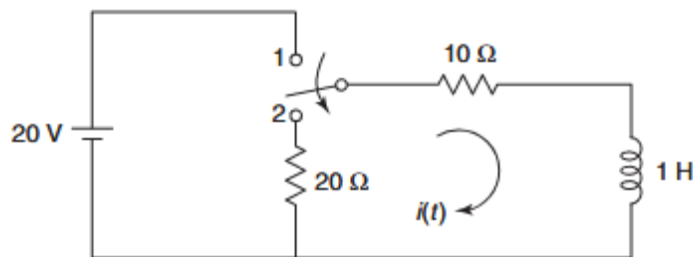


- b. Find h parameters for the following network. State whether given network is reciprocal or not.

(10)

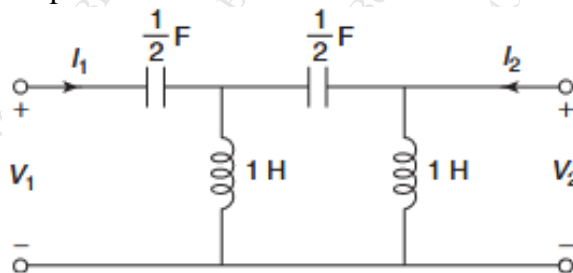


**Q4.** Solve the following

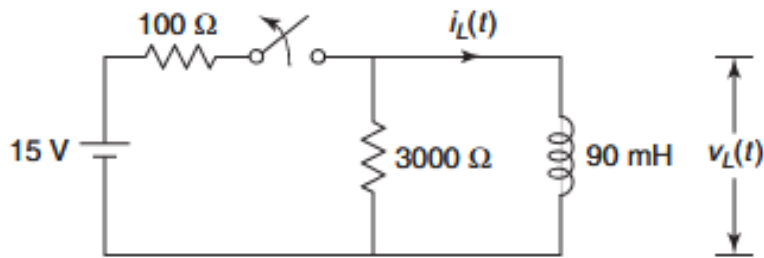- a. Steady state is reached with the switch closed. The switch is opened at  $t = 0$ . Obtain expressions for  $i_L(t)$  Obtain the expression (10)




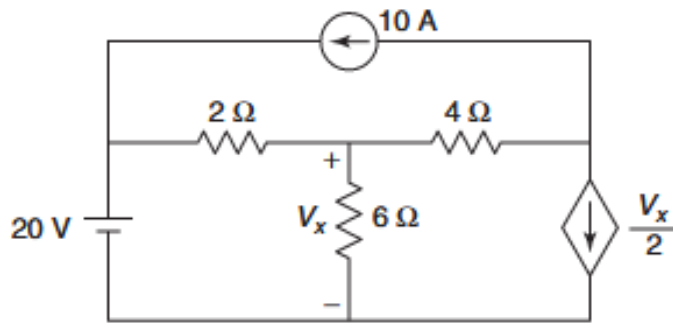- b. Find the voltage  $V_x$  using superposition theorem (10)




**Q5.** Solve the following

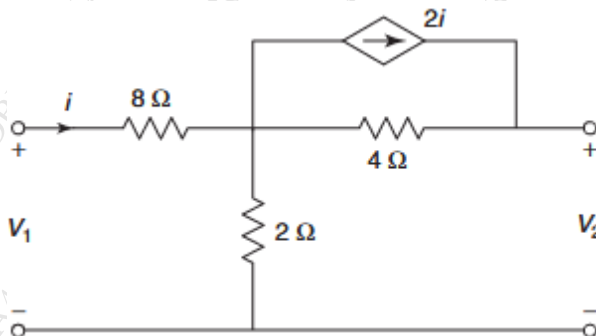- a. Find the Y parameters for the network shown (10)




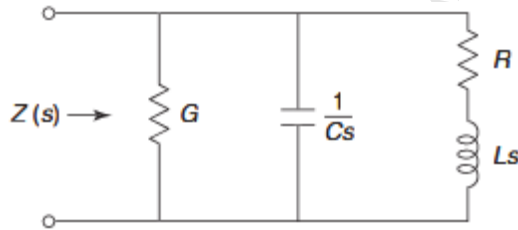- b. A driving-point impedance  $Z(s)$  for the network is as shown. Calculate the values of the parameters  $R$ ,  $L$ ,  $G$  and  $C$  if  $Z(j0) = 1$ . The poles are located at  $-3 \pm j3$  and zero at  $-2$  (10)



Q6. Solve the following

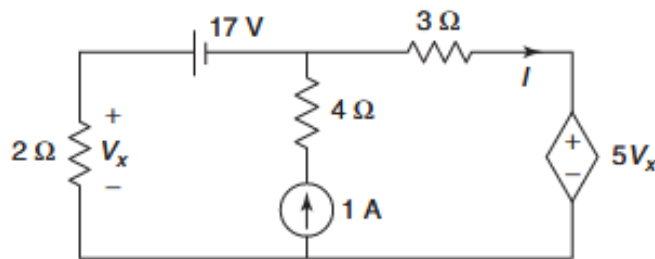- a. Find the current  $I$  using supermesh theorem (10)



- b. For the network shown, determine  $Z_{11}(s)$ ,  $G_{12}(s)$  and  $Z_{12}(s)$  (10)

