

Time: 3 HRS

Marks: 80

Note: 1) Question No. 1 is compulsory.

2) Solve any three questions out of remaining five questions.

3) Assume suitable data if necessary.

4) Figures to the right indicate full marks.

- 1** Answer any **four**. **20**
- Compare three modes of transistor operation based on biasing conditions of each junction and their application.
 - Perform $(89)_{10} - (26)_{10}$ using 2's complement method.
 - With neat circuit diagram and truth table explain 2:4 Decoder.
 - Draw circuit diagram of positive edge triggered T flip-flop and write its function table.
 - Design half adder using logic gates.
- 2** a) Explain working operation of current mirror circuit with its circuit diagram. **10**
 b) Using K-map get the minimal SOP equation for the given function F and draw logic circuit for the minimized equation using different logic gates. **10**

$$F(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 9, 10, 11, 12, 15).$$
- 3** a) Design a 3 bit binary synchronous up-counter using negative edge triggered D Flip-flop. **10**
 b) Implement the following logic function using 8:1 MUX and few logic gates. **10**

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 7, 9, 10, 13, 15)$$
- 4** a) What is shift register? With neat diagram explain working operation of 3-bit Serial Input Parallel Output (SIPO) shift right register. **10**
 b) Explain VHDL Program format and write VHDL program for full adder. **10**
- 5** a) Simplify the following equation using Boolean algebra and design simplified function using basic logic gates. **10**

$$F(A, B, C) = AB + \overline{A}\overline{C} + A\overline{B}C(A + C)$$

 b) Explain working of operation of ring counter with its circuit diagram. **10**
- 6** Answer any **four**. **20**
- Explain differential amplifier with diagram
 - Working operation of negative edge triggered D flip-flop with circuit diagram.
 - Working of 4:1 Multiplexer with truth table and circuit diagram.
 - Covert hexadecimal number $(8E)_{16}$ to binary, octal, decimal and gray code.
 - Draw and explain one digit BCD adder.