

**Instructions:**Total Time: **3 Hrs**Total Marks: **80**

1. Question No: **1** is **compulsory**.
2. Answer any **three** from the **remaining five** questions.
3. Figures to the right indicate full marks.

- |          |   |             |
|----------|---|-------------|
| <b>1</b> | Solve <b>any four</b> :-  | <b>(20)</b> |
|          | a) Draw application circuit of triac-diac and associated waveforms.   |             |
|          | b) Enlist applications of inverter?   |             |
|          | c) Draw buffer, integrator and Schmitt trigger circuit.   |             |
|          | d) Define and describe logic operation, power dissipation and propagation delay in digital circuits.          |             |
|          | e) Draw and explain generic microcontroller.  |             |
| <b>2</b> | a) Describe speed torque characteristics of dc and ac motors.   | <b>(07)</b> |
|          | b) Explain three phase inverter operation with waveforms.   | <b>(07)</b> |
|          | c) Describe in detail instrumentation amplifier. State its need and applications.                             | <b>(06)</b> |
| <b>3</b> | a) Explain an ac to dc converter supplying resistive load. Derive equation for calculating dc voltage.        | <b>(07)</b> |
|          | b) Explain procedure to select a motor for an application and describe with the speed torque characteristics. | <b>(07)</b> |
|          | c) Explain in detail low pass active filter   | <b>(06)</b> |
| <b>4</b> | a) Explain need of digital to analogue conversion. How the ADC in MSP430 works?                               | <b>(07)</b> |
|          | b) Compare analogue and digital circuits. Enlist some of them.  | <b>(07)</b> |
|          | c) Describe closed loop speed control of DC motor.  | <b>(06)</b> |
| <b>5</b> | a) Draw and explain architecture MSP 430 microcontroller?   | <b>(07)</b> |
|          | b) What is MOSFET? Explain its working. What are similarities between MOSFET and IGBT?                        | <b>(07)</b> |
|          | c) Explain IC 555 timer as Monostable Multivibrator.  | <b>(06)</b> |
| <b>6</b> | a) Explain with circuit diagram any forced commutation method of SCR.   | <b>(07)</b> |
|          | b) Compare microprocessor and microcontroller.  | <b>(07)</b> |
|          | c) Explain Demultiplexer and Decoder.   | <b>(06)</b> |