

**Duration: 3Hrs.**

**[Max Marks:80]**

**N.B.: (1) Question No 1 is Compulsory.**

**(2) Attempt any three questions out of the remaining five.**

**(3) All questions carry equal marks.**

**(4) Assume suitable data, if required and state it clearly.**

- 1 Attempt any FOUR [20]**
  - a Write note on BLDC Motor. [05]**
  - b What is the necessity of inner current loop control circuit for speed control of DC motor [05]**
  - c Draw and explain Architecture of generic microprocessor. [05]**
  - d Draw and explain Low Pass Filter. [05]**
  - e Realize X-OR gate by NAND gate. [05]**
- 2 a With neat circuit diagram and waveforms, explain single phase full wave half controlled rectifier circuit supplying a resistive load [10]**
  - b Draw V-I characteristic of SCR and Explain any one force commutation method of SCR. [10]**
- 3 a What is MOSFET? Explain its working .What are similarities between MOSFET and IGBT?. [10]**
  - b Draw and explain the working of multiplexer and de- multiplexer. [10]**
- 4 a Explain with the help of a neat circuit diagram how diac can be used to trigger a traic. What are the applications of this circuit? [10]**
  - b What are similarities and dissimilarities of microprocessor and micro-controller ? [10]**
- 5 a List various speed control methods of induction motor. Explain voltage control method with a suitable diagram. [10]**
  - b Explain the working principle of single phase bridge inverter circuit. [10]**
- 6 a What are inverting and non-inverting amplifiers? Write their gain equations. Draw the circuit diagram for OPAMP as summing amplifier and also write its output voltage equation. [10]**
  - b Draw and explain functional diagram of MSP430 micro-controller. [10]**

\*\*\*\*\*