

Marks : 80]

Time : 3 Hours

Marks : 80

N.B: (1) Question no.1 is compulsory

(2) Solve any three from remaining questions

(3) Assume suitable data if necessary

(4) Figures to the right indicate full marks

1. Solve any four: 20
 - (a) Compare ideal and Practical op-amp.
 - (b) Explain working principle of GTO and Compare it with SCR..
 - (c) Realize derived gates using NAND gate.
 - (d) Explain importance of Back EMF in D.C motors.
 - (e) Discuss effect RLE load on full wave rectifier operation.
 2. (a) Explain working of inverter circuit? Identify its type and explain any one. 7
 - (b) Select motors for medium power pump and conveyor applications 7
 - (c) Compare power BJT and Power MOSFET 6
 3. (a) Explain single phase full wave fully controlled rectifier circuit supplying a resistive load. 7
 - (b) Explain with neat Block Diagram architecture of MSP430 microcontroller 7
 - (c) Describe in detail Op-amp as a Summing Amplifier. 6
 4. (a) Give Significance of Inner current loop control circuit. 7
 - (b) Explain basic circuit of IC 555. 7
 - (c) What is Commutation in SCR and Explain its working principle. 6
 5. (a) Explain with detailed circuit diagram any one application circuit of TRIAC-DIAC pair. 7
 - (b) Compare with examples combinational and sequential circuits. 7
 - (c) Compare Microprocessor and Microcontroller. 6
 6. (a) Enlist register related to configuration of digital input/output port of MSP 430 microcontroller. And explain their importance. 7
 - (b) What is a servomotor? What are the requirements of a good servomotor? 7
 - (c) What do you understand by a digital circuit? Explain various parameters of logic family. 6
-